

Unit 4: Application of Boolean Algebra Midterm and Maxterm Expansions

4.1 Conversion of English Sentences to Boolean Equations.

3 steps to design a single output combinational switching circuit

- 1) Find a switching function that specifies the desired behavior (OR, AND, etc.)
- 2) Find a simplified algebraic expression
- 3) Realize the simplified function using available logic elements

Ex 1) Mary watches TV if it is Monday night and she has finished her homework

3 phrases with two variables

F = 1, Mary watches TV	F = 0 otherwise
A = 1, it is Monday night	A = 0 otherwise
B = 1, she has finished her hw	B = 0 otherwise

Because F is true if A and B are both true, we can write

$$F = A \cdot B$$

Ex 2) The alarm will ring iff the alarm switch is turned on and the door is not closed or it is after 6 pm and the window is not closed


5 phrases

Z = 1, the alarm will ring
A = 1, alarm switch is on
B' = 1, the door is not closed
C = 1, it is after 6 pm
D' = 1, window is not closed

$$Z = A \cdot B' + C \cdot D'$$

Circuit form

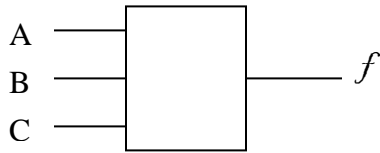4.2 Combinational Logic Design Using a Truth Table



Where A, B, and C represent 1st, 2nd, and 3rd bits respectively of number N
 $f = 1$ for $N \geq 011_2$ and $f = 0$ for $N < 011_2$

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

Derive equation for values of $f = 1$

$$f = A' B C + A B' C' + A B' C + A B C' + A B C$$

Simplifying,

$$A' B C + A B' (C' + C) + A B (C + C') =$$

$$A' B C + A B' + A B =$$

$$A' B C + A (B' + B) =$$

$$A' B C + A =$$

$$A + BC$$

Note:

$$(y + y' x) = x + y$$

Can also solve by representing $f = 0$

$$f = (A + B + C) (A + B + C') (A + B' + C)$$

Can also solve by representing $f' = 1$ then take the complement to get f

$$f' = A' B' C' + A' B' C + A' B C'$$

Take the complement to get f :

$$(f')' = (A' B' C')' (A' B' C)' (A' B C')'$$

$$f = (A + B + C) (A + B + C') (A + B' + C)$$

$$f = (A + B) (A + B' + C)$$

$$f = A + B (B' + C)$$

$$f = A + BC$$

$$(x+y)(x+y')=x$$

$$x=A, y=B, z= B'+ C$$

4.3 Minterm and Maxterm Expansions

Minterm: term of n variables which is a product of n literals in which each variable appears exactly once in either true or complemented form, but not both.

Row	A	B	C	Minterms
0	0	0	0	$A'B'C' = m_0$
1	0	0	1	$A'B'C = m_1$
2	0	1	0	$A'BC' = m_2$
3	0	1	1	$A'BC = m_3$
4	1	0	0	$AB'C' = m_4$
5	1	0	1	$AB'C = m_5$
6	1	1	0	$ABC' = m_6$
7	1	1	1	$ABC = m_7$

Each minterm has a value of 1 for exactly one combination of values of the variables A, B and C.

If $A = B = C = 0$ then $A' B' C' = 1$ and is designated as m_0

$f = A' B C + A B' C + A B' C' + A B C' + A B C$ is an example of a function written as a sum of minterms. It is often referred to as minterm expansion or standard sum of products.

The above equation can be rewritten in m-notation,

$$f(A, B, C) = m_3 + m_4 + m_5 + m_6 + m_7$$

$$f(A, B, C) = \Sigma m (3,4,5,6,7)$$

Maxterm: term of n variables which is a sum of n literals in which each variable appears exactly once in its true or complemented form, but not both.

Row	A	B	C	Maxterms
0	0	0	0	$A+B+C = M_0$
1	0	0	1	$A+B+C' = M_1$
2	0	1	0	$A+B'+C = M_2$
3	0	1	1	$A+B'+C' = M_3$
4	1	0	0	$A'+B+C = M_4$
5	1	0	1	$A'+B+C' = M_5$
6	1	1	0	$A'+B'+C = M_6$
7	1	1	1	$A'+B'+C' = M_7$

Each maxterm has a value of zero for exactly one combination of values of A, B, and C. Thus $A = B = C = 0$ $A + B + C = 0$ and is designated M_0

Note: The maxterm is the complement of the corresponding minterm

$f = (A + B + C) (A + B + C') (A + B' + C)$ is an example of a function written as a product of maxterms. Referred to as maxterm expansion or standard product of sums

Rewritten in M-notation,
 $f(A, B, C) = M_0 M_1 M_2$

Abbreviated
 $f(A, B, C) = \Pi M (0, 1, 2)$

In general, switching expressions can be converted to minterm or maxterm expansions either by using a truth table or algebraically.

Note: Another way to obtain the minterm expansion is to first write the expression as a sum of products and introduce missing variables in each term by applying $x + x' = 1$

Ex) Find minterm expansion of $f = (a, b, c, d) = a' (b' + d) + acd'$

$$= a'b' + a'd + acd'$$

$$= a'b'(c + c')(d + d') + a'd(b + b')(c + c') + acd'(b + b')$$

$$= a'b'cd + a'b'cd' + a'b'c'd + a'b'c'd' + a'bcd + a'bc'd + a'b'cd + a'b'cd' + abcd' + ab'cd'$$

$$= a'b'c'd' + a'b'c'd + a'b'cd' + a'b'cd + a'bc'd + a'b'c'd + abcd' + ab'cd'$$

Decimal notation,

a'b'c'd'	a'b'c'd	a'b'cd'	a'b'cd	a'bc'd	a'b'c'd	abcd'	ab'cd'
0000	0001	0010	0011	0101	0111	1110	1010

$$f(a, b, c, d) = \Sigma m(0, 1, 2, 3, 5, 7, 10, 14)$$

Maxterms: ones not listed in minterm for n = 4

$$f(a, b, c, d) = \Pi M(4, 6, 8, 9, 11, 12, 13, 15)$$

Alternate method for maxterm: Factor f to obtain product of sums and introduce missing variables using $xx' = 0$ then factor again for maxterm

$$f = a'(b' + d) + acd'$$

x' z x y

$$= [a + (b' + d)] (a' + cd')$$

x yz

$$= (a + b' + d) (a' + c) (a' + d')$$

$$= (a + b' + cc' + d) (a' + bb' + c + dd') (a' + bb' + cc' + d')$$

$$= (a + b' + c + d) (a + b' + c' + d) (a' + bb' + c + d) (a' + bb' + c + d')$$

$$(\cancel{a' + bb' + c + d'}) (a' + bb' + c' + d')$$

$$= (a + b' + c + d) (a + b' + c' + d) (a' + b + c + d) (a' + b' + c + d) (a' + b + c + d')$$

$$(a' + b' + c + d') (a' + b + c' + d') (a' + b' + c' + d')$$

$$= (a + b' + c + d) (a + b' + c' + d) (a' + b + c + d) (a' + b' + c + d) (a' + b + c + d')$$

0100 0110 1000 1100 1001

$$(a' + b' + c + d') (a' + b + c' + d') (a' + b' + c' + d')$$

1101 1011 1111

$$f = \Pi M(4, 6, 8, 9, 11, 12, 13, 15)$$

Note: in maxterm translation to decimal, primed values equate to a 1 and nonprimed to a zero

An equation can be proven valid by factoring the minterm expansions of each side and showing the expansions are the same

Ex) $a'c + b'c' + ab = a'b' + bc + ac'$

Left side,
 $= a'c (b + b') + b'c' (a + a') + ab (c + c')$

$$= a'bc + a'b'c + ab'c' + a'b'c' + abc + abc'$$

$$\quad 011 \quad 001 \quad 100 \quad 000 \quad 111 \quad 110$$

$$= m_3 + m_1 + m_4 + m_0 + m_7 + m_6$$

Right side,
 $= a'b' (c + c') + bc(a + a') + ac' (b + b')$

$$= a'b'c + a'b'c' + abc + a'bc + abc' + ab'c'$$

$$\quad 001 \quad 000 \quad 111 \quad 011 \quad 110 \quad 100$$

$$= m_1 + m_0 + m_7 + m_3 + m_6 + m_4$$

4.4 General Minterm and Maxterm Expansions

A	B	C	F
0	0	0	a ₀
0	0	1	a ₁
0	1	0	a ₂
0	1	1	a ₃
1	0	0	a ₄
1	0	1	a ₅
1	1	0	a ₆
1	1	1	a ₇

For a function n, there are 2ⁿ rows of a truth table and 2^{2ⁿ} possible functions of n variables.

Minterm expansion for a general function (3 variables)

$$F = a_0m_0 + a_1m_1 + a_2m_2 + \dots + a_7m_7 = \sum_{i=0}^7 (a_i m_i)$$

Maxterm expansion for a general function

$$F = (a_0 + m_0) (a_1 + m_1) (a_2 + m_2) \dots (a_z + m_z) = \prod_{i=0}^7 (a_i + m_i)$$

Generalized

$$F = \sum_{i=0}^{2^n-1} a_i m_i = \prod_{i=0}^{2^n-1} (a_i + m_i)$$

$$F' = \sum_{i=0}^{2^n-1} a_i' m_i = \prod_{i=0}^{2^n-1} (a_i' + m_i)$$


Given two different minterms of n variable $m_i + m_j$ at least one variable appears complemented in one minterm and in uncomplemented in the other.

Therefore if $i \neq j$ $m_i m_j = 0$

Ex) $f_1 = \sum m(0, 2, 3, 5, 9, 11)$ $f_2 = \sum m(0, 3, 9, 11, 13, 14)$

$$f_1 f_2 = \sum m(0, 3, 9, 11)$$

4.5 Incompletely Specified Functions

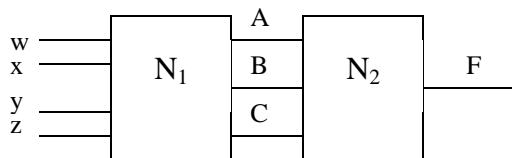

Assume that the output of N_1 has no combination of values for w , x , y , and z to cause A , B , and C to have a value of 001 and 110 . Then when designing N_2 it is not necessary to specify values of F for $ABD = 001$ and 110 .

A	B	C	F
0	0	0	1
0	0	1	X
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X
1	1	1	1

The X's indicate "don't cares" because the values could be 0 or 1 since they will never occur anyway. A function in this format is said to be incompletely specified.

To realize a function, a value must be specified for the “don’t cares”. It is best to choose a value that helps to simplify the function.

Example for both $X = 0$;

$$\begin{aligned} F &= A'B'C' + A'BC + ABC \\ &= A'B'C' + BC(A' + A) \\ &= A'B'C' + BC \end{aligned}$$

Example for first $X = 1$ and second $X = 0$;

$$\begin{aligned} F &= A'B'C' + A'B'C + A'BC + ABC \\ &= A'B'(C' + C) + BC(A' + A) \\ &= A'B' + BC \end{aligned}$$

Example for both $X = 1$;

$$\begin{aligned} F &= A'B'C' + A'B'C + A'BC + ABC' + ABC \\ &= A'B'(C' + C) + BC(A' + A) + ABC' \\ &= A'B' + B(C + AC') && (Y + XY' = X + Y) \\ &= A'B' + B(C + A) \end{aligned}$$

(The second example yields the simplest solution.)

Minterm expansion for incompletely specified functions; where m = minterm & d = don’t cares

$$F = \sum m(0, 3, 7) + \sum d(1, 6)$$

Maxterm expansion for incompletely specified functions; where M = Maxterm & D = don’t cares

$$F = \prod M(2, 4, 5) \cdot \prod D(1, 6)$$

4.6 Examples of Truth Table Construction

Example 1) Design a binary adder using two 1-bit binary numbers

a	b	Sum	
0	0	0 0	(0 + 0 = 0)
0	1	0 1	(0 + 1 = 1)
1	0	0 1	(1 + 0 = 1)
1	1	1 0	(1 + 1 = 2)

Construct a truth table with logic variables A and B and 2-bit sum logic variables x and y

A	B	X	Y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Because numeric zero is represent by logic zero and numeric 1 by logic 1,

$$X = AB \quad \text{and} \quad Y = A'B + AB' = A \oplus B$$

Example 2) Adder of two 2-bit binary numbers to form a 3-bit sum

N₁		N₂		N₃		
A	B	C	D	X	Y	Z
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Output function:

$$X(A, B, C, D) = \Sigma m(7, 10, 11, 13, 14, 15)$$

$$Y(A, B, C, D) = \Sigma m(2, 3, 5, 6, 8, 9, 12, 15)$$

$$Z(A, B, C, D) = \Sigma m(1, 3, 4, 6, 9, 11, 12, 14)$$

Example 3) Design an error detector for 6-3-1-1 BCD digit. $F = 1$ iff if the four digits (A, B, C, D) are an invalid code. (page 21)

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Output

$$F(A, B, C, D) = \Sigma m(2, 6, 10, 13, 14, 15)$$

$$= A'B'CD' + A'BCD' + AB'CD' + ABCD' + ABC'D + ABCD$$

$$= A'CD'(B + B') + ACD'(B + B') + ABD(C + C')$$

$$= A'CD' + ACD' + ABD$$

$$= CD' + ABD$$

Circuit Equation:

Example 4) Design a circuit for an 8-4-2-1 BCD digit (A, B, C, D) where $Z = 1$ if the decimal is exactly divisible by 3.

0, 3, 6 and 9 are divisible by 3 while 10 – 15 are not valid. (See page 21.)

A	B	C	D	Z
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Output:

$$F(A,B,C,D) = \sum m (0,3,6,9) + \sum d (10,11,12,13,14,15)$$

To simplify, the easiest solution is a Karnaugh Map which is covered in Unit 5

4.7 Design of Binary Adders and Subtractors

Adders:

Design a parallel adder that adds two 4-bit unsigned binary numbers and a carry input to give a 4-bit sum and carry output.

Option 1: Use a truth table to design the adder ... this is very difficult

Option 2: Design a module for a 2-bit adder with a carry (Full Adder).

Then connect four together to form a 4-bit adder.

Truth Table

X	Y	C_{in}	C_{out}	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Logic Equation:

$$\begin{aligned}\text{Sum} &= X'Y'C_{in} + X'YC_{in}' + XYC_{in}' + XYC_{in} \\ &= X'(Y'C_{in} + YC_{in}') + X(Y'C_{in}' + YC_{in}) \\ &= X'(Y \oplus C_{in}) X(Y \oplus C_{in})' \\ &= X \oplus (Y \oplus C_{in}) \\ &= X \oplus Y \oplus C_{in}\end{aligned}$$

$$\begin{aligned}C_{out} &= X'YC_{in} + XY'C_{in} + XYC_{in}' + XYC_{in} \\ &= (X'YC_{in} + XYC_{in}) + (XY'C_{in} + XYC_{in}) + (XYC_{in}' + XYC_{in}) \\ &= YC_{in}(X' + X) + XC_{in}(Y' + Y) + XY(C_{in}' + C_{in}) \\ &= YC_{in} + XC_{in} + XY\end{aligned}$$

Circuit Equation:

Adders for signed numbers: negatives expressed in complement form.

2's complement – the last carry is discarded

1's complement – the last carry is end around carry

Overflow – when two positive numbers yield a negative number
– when two negative numbers yield a positive number

Subtractors: Accomplished by adding the complement of the number to be subtracted.
Use either 1's or 2's complement.

Another method is to employ a full subtractor

Where x_i , y_i and b_i are inputs; b_{i+1} and d_i are outputs (b = borrow, d = difference)

Truth Table

x_i	y_i	b_i	b_{i+1}	d_i
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1