

## Chapter 2: Circuit Elements

### 2.1 Voltage and Current Sources

Electrical source: device capable of converting nonelectric energy to electrical energy (battery); is an active element

Active element: models a physical device capable of generating electrical energy

Passive element: models a physical device that is not capable of generating electrical energy (resistor, capacitor, inductor, etc.)

Ideal voltage source: a circuit element that maintains a prescribed voltage regardless of the current in the device


Ideal current source: a circuit element that maintains a prescribed current regardless of the voltage across the device

Note: For an ideal voltage source it is not possible to specify the current as a function of its voltage; for an ideal current source it is not possible to specify the voltage as a function of its current.

#### 2 Types of Sources

Independent: not influenced by other currents or voltages in the circuit

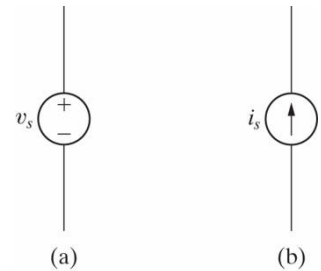
- (a) an ideal voltage source
- (b) an ideal current source



Dependent: determined by some other current or voltage in the circuit

The circuit symbols for:

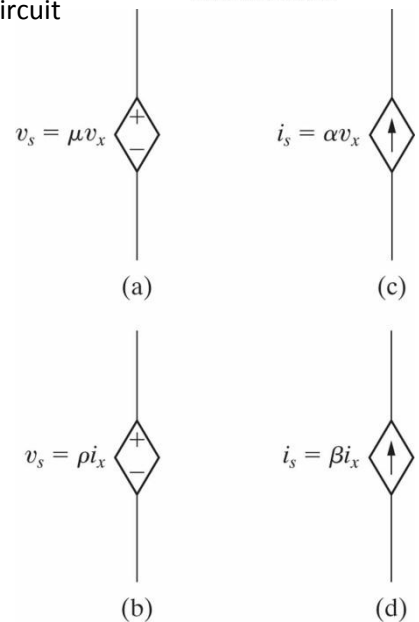- (a) an ideal dependent voltage-controlled voltage source
- (b) an ideal dependent current-controlled voltage source
- (c) an ideal dependent voltage-controlled current source
- (d) an ideal dependent current-controlled current source.



Where  $v_x$  and  $i_x$  are the controlling voltage and current

And  $\mu$ ,  $\alpha$ ,  $\rho$  and  $\beta$  are multiplying constants

*Review Example Problems 2.1 & 2.2 and Assessment Problems 2.1 & 2.2*

### 2.2 Electrical Resistance (Ohm's Law)

Resistance: capacity of materials to impede the flow of electric charge

## Chapter 2: Circuit Elements



**Resistor:** circuit element used to model the behavior of resistance

### Ohm's Law

$$v = iR$$

Where  $v$  = voltage in volts;  $i$  is the current in amps;  $R$  is the resistance in ohms

Rewriting

$$i = \frac{v}{R}$$

Given

$$p = vi = (iR)i = i^2R$$


$$p = vi = v\left(\frac{v}{R}\right) = \frac{v^2}{R}$$

The reciprocal of resistance is *conductance* measured in Siemens

$$G = \frac{1}{R}S$$

Thus

$$p = v^2G = \frac{i^2}{G}$$

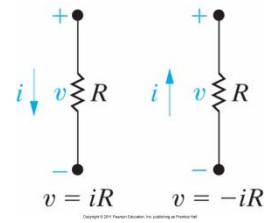

*Review Example Problem 2.3 and Assessment Problems 2.3 & 2.4*

### 2.3 Construction of a Circuit Model

General observations about modeling

- Electrical behavior of each component is of primary interest
- Models need to account for both desired and undesired electrical effects (heat from a light)
- Modeling requires approximations (ignore resistance inherent in some elements)

*Example 2.4 – Circuit model for a flashlight*

Analyzing:

Battery – ideal voltage source ( $v_s$ )

Lamp – resistor ( $R_l$ )

Switch

Lamp connection – resistor ( $R_1$ )

Case connection – resistor ( $R_1$ )





Short circuit ( $R=0$ )



Open Circuit ( $R=\infty$ )




Switch

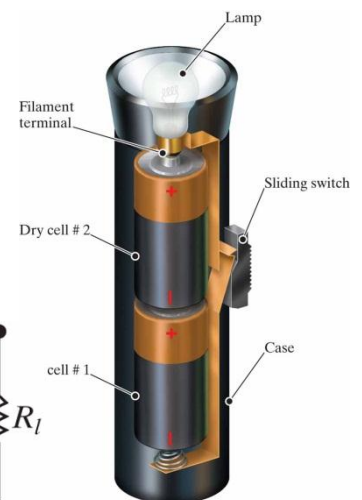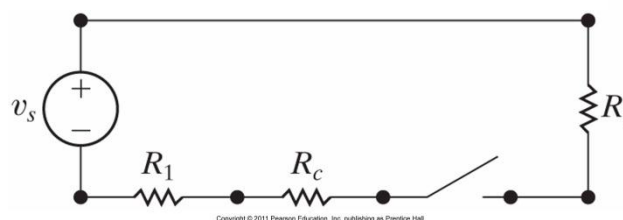

## Chapter 2: Circuit Elements

### Example 2.5

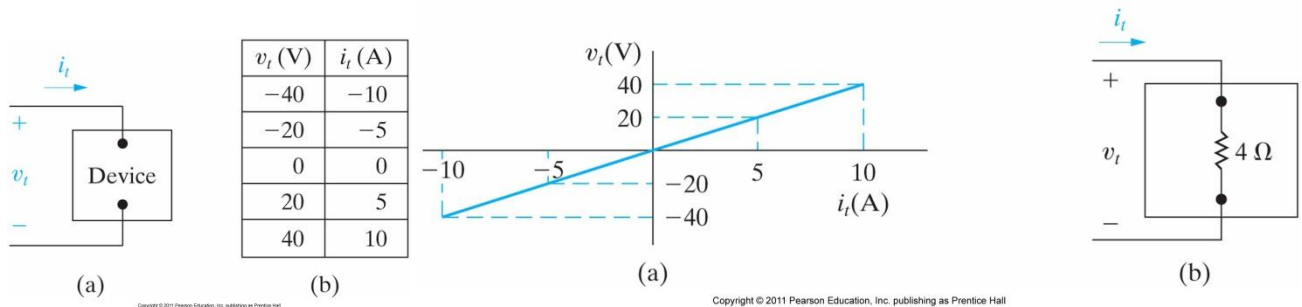


### 2.4 Kirchhoff's Law

**Node:** a point where two or more circuit elements meet

**Kirchhoff's Current Law (KCL):** the algebraic sum of all the currents at any node in a circuit equals zero.

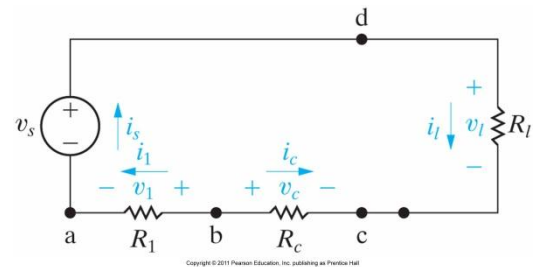First a sign for each direction of the current must be assigned: (positive for current leaving a node; negative when entering) (negative for current leaving a node; positive when entering)



From the circuit we obtain the following node equations

$$(a) \ i_s - i_1 = 0 \qquad (b) \ i_1 + i_c = 0 \qquad (c) \ -i_c - i_l = 0 \qquad (d) \ i_l - i_s = 0$$

Note: for a circuit containing n nodes; n-1 independent current equations can be derived.

**Closed loop/path:** beginning at any node, trace a closed path in a circuit through selected basic circuit elements and return to the original node without passing through any intermediate node more than once

**Kirchhoff's Voltage Law (KVL):** the algebraic sum of all the voltages around a closed path in a circuit equals zero.

First a sign for each voltage must be assigned: (positive for a voltage rise; negative for a voltage drop) (negative for a voltage rise; positive for a voltage drop)


For the circuit starting at node d and tracing a closed path yields:

$$v_l - v_c + v_1 - v_s = 0$$

#### Observations


- If you know either the voltage across or current through a resistor you can determine the other by using Ohm's Law
- When only two elements are connected to a node, if you know the current in one element you know the current in the other. The elements are said to be connected in *series*.

Example 2.6 – Using KCL

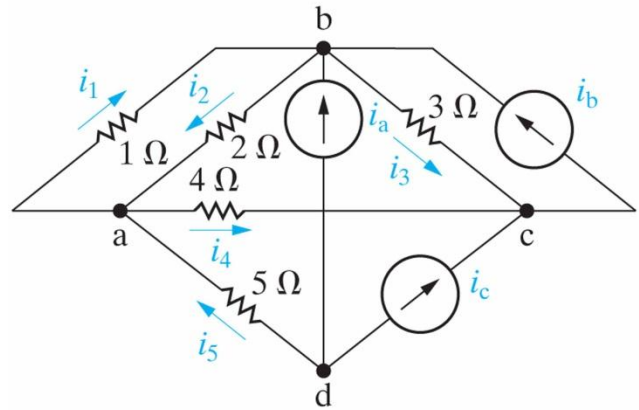

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


Example 2.7 – Using KVL

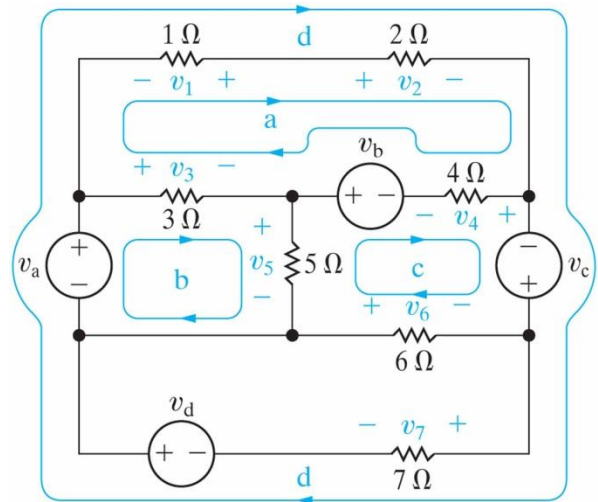

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Review Examples 2.8 & 2.9 and Assessment Problems 2.5 – 2.8

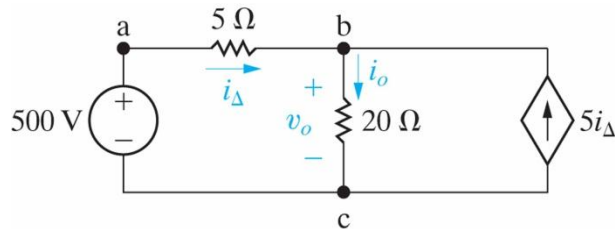2.5 Analysis of a Circuit Containing Dependent Sources



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Using Kirchhoff's Laws and Ohm's Law to find  $v_o$

- To determine the voltage we must find the two currents.
- KVL for the left path:

$$500 = 5i_{\Delta} + 20i_o$$

KCL at the top node:

$$5i_{\Delta} + i_{\Delta} = i_o = 6i_{\Delta}$$

Substituting and solving

$$i_{\Delta} = 4 \text{ A}$$

$$i_o = 24 \text{ A}$$

Review Example Problems 2.10 & 2.11 and Assessment Problems 2.9 & 2.10