
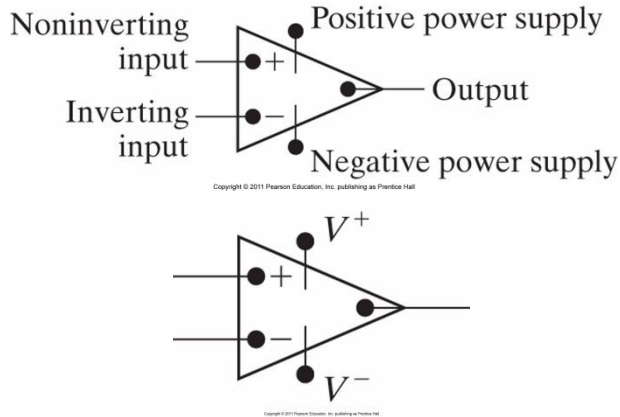


5.1 Operational Amplifier Terminals

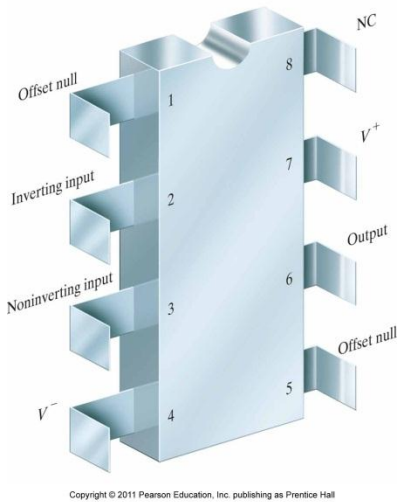

5.2 Terminal Voltages and Currents

All voltages are considered as a voltage rise from the common node.

$V_{CC}$  = positive voltage supply     $-V_{CC}$  = negative voltage supply

$v_n$  = voltage between inverting terminal and common node

$v_p$  = voltage between noninverting terminal and common node

$v_o$  = voltage between output terminal and common node

$i_n$  = current into the inverting terminal

$i_p$  = current into the noninverting terminal




$i_o$  = current into the output terminal

$i_{c+}$  = current into the positive power supply terminal

$i_{c-}$  = current into the negative power supply terminal

Characteristics:
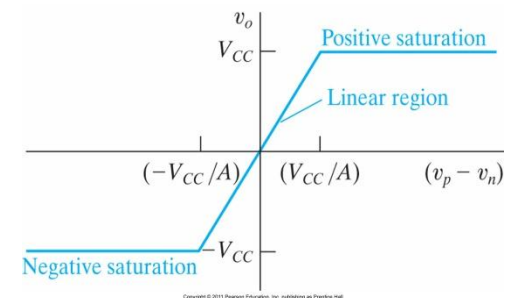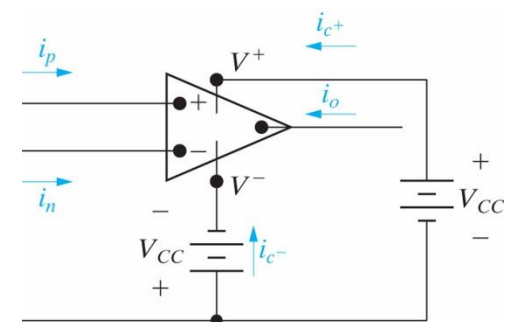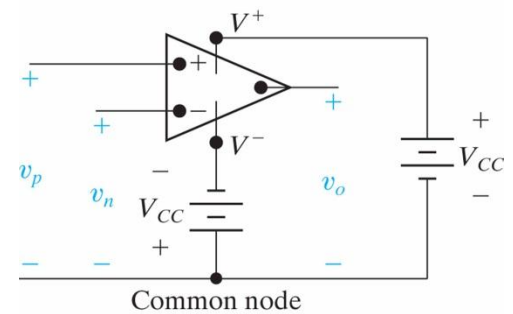
$$v_o = \begin{cases} -V_{CC}, & A(v_p - v_n) < -V_{CC} \\ A(v_p - v_n), & -V_{CC} \leq A(v_p - v_n) \leq +V_{CC} \\ +V_{CC}, & A(v_p - v_n) > +V_{CC} \end{cases}$$



Where A is the **gain**

Input voltage constraint for an ideal op-amp  $v_p = v_n$  ; when in its linear range

Negative feedback: output signal fed back into the inverted output (w/out neg. fb op-amp usually saturates)

## Chapter 5: The Operational Amplifier


Input current constraint for an ideal op-amp  $i_p = i_n = 0$

KCL around the op-amp

$$i_p + i_n + i_o + i_{c+} + i_{c-} = 0$$

$$i_o = -(i_{c+} + i_{c-})$$

### Example 5.1

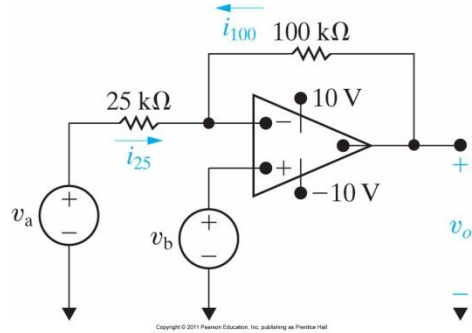

For ideal,  $i_p = i_n = 0$  and  $v_p = v_n$  if in linear range

- a)  $v_a = 1V$  and  $v_b = 0V$
- b)  $v_a = 1V$  and  $v_b = 2V$
- c)  $v_a = 1.5V$  and  $v_b = ??$

Note: negative feedback so assume linear region

▼ Part a. KCL

$$i_n - i_{25} - i_{100} = 0 \quad \text{yields} \quad i_n = i_{25} + i_{100} = 0$$

Ohm's

$$i_{25} = \frac{v_a - v_n}{25k} = \frac{1 - 0}{25k} = \frac{1}{25} mA$$

$$i_{100} = \frac{v_o - v_n}{100k} = \frac{v_o - 0}{100k} = \frac{v_o}{100k} = -\frac{1}{25} mA$$

$$v_o = -4V$$

Part b.

$$i_{25} = \frac{v_a - v_n}{25k} = \frac{1 - 2}{25k} = -\frac{1}{25} mA$$

$$i_{100} = \frac{v_o - v_n}{100k} = \frac{v_o - 2}{100k} = -\frac{1}{25} mA$$

$$v_o = 6V$$

Part c.

$$\frac{v_a - v_n}{25k} = -\frac{v_o - v_n}{100k}$$

$$v_n = v_b = \frac{1}{5}(6 + v_o)$$

For linearity  $-10V \leq v_o \leq 10V$

Therefore

$$-0.8 \leq v_b \leq 3.2V$$

Review Assessment Problem 5.1

5.3 The Inverting-Amplifier Circuit

$$i_s + i_f = i_n = 0$$

$$i_s = \frac{v_s}{R_s} \quad i_f = \frac{v_o}{R_f}$$

$$v_o = \frac{-R_f}{R_s} v_s \quad \text{where } \frac{R_f}{R_s} \text{ is the gain}$$

Assuming the power supply voltages are equal;



$$|v_o| \leq V_{CC}, \quad \left| \frac{R_f}{R_s} v_s \right| \leq V_{CC}, \quad \frac{R_f}{R_s} \leq \left| \frac{V_{CC}}{v_s} \right|$$

Open loop removing the feedback branch from the op amp

$$v_o = -A v_n \quad \text{where } v_n \approx v_s$$

For linear operation  $|v_s| < \frac{V_{CC}}{A}$

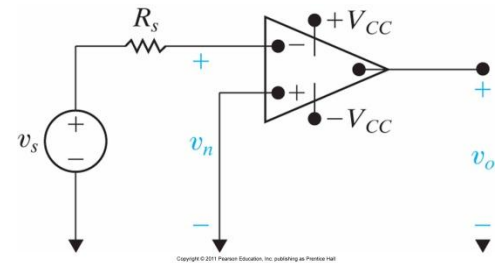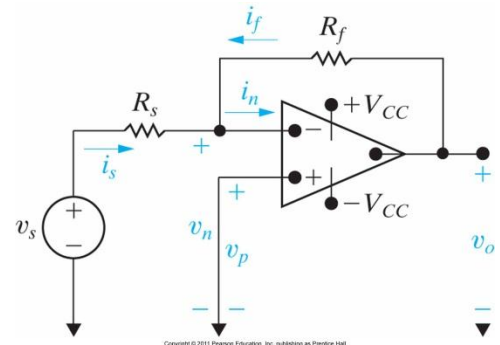Review Example 5.2 and Assessment Problem 5.2



5.4 The Summing-Amplifier Circuit

$$\frac{v_n - v_a}{R_a} + \frac{v_n - v_b}{R_b} + \frac{v_n - v_c}{R_c} + \frac{v_n - v_o}{R_f} + i_n = 0$$

Assuming an ideal op amp

$$v_o = - \left( \frac{R_f}{R_a} v_a + \frac{R_f}{R_b} v_b + \frac{R_f}{R_c} v_c \right)$$

If  $R_a = R_b = R_c = R_s$

$$v_o = - \frac{R_f}{R_s} (v_a + v_b + v_c)$$

If  $R_f = R_s$

$$v_o = -(v_a + v_b + v_c)$$

Note: The summing op amp can have any number of input voltages applied to it for summing

Review Assessment Problem 5.3



5.5 The Noninverting-Amplifier Circuit

The voltage source is applied to the positive terminal of the op amp

$$v_n = v_p \approx v_g$$

$$\frac{v_n}{R_s} + \frac{v_n - v_o}{R_f} + 0 = 0$$
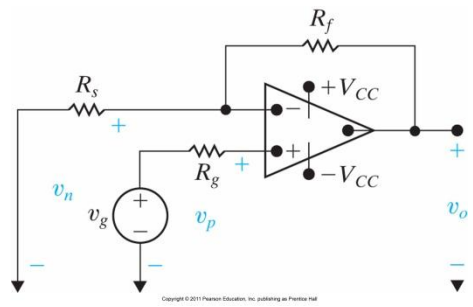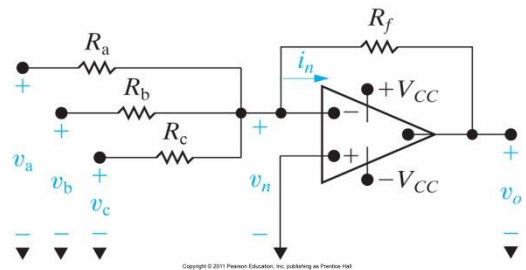
$$v_o = \left( \frac{R_f + R_s}{R_s} \right) v_g$$



## Chapter 5: The Operational Amplifier

The op amp operates in the linear region when  $\frac{R_f + R_s}{R_s} < \frac{V_{CC}}{v_g}$

Review Example 5.3 and Assessment Problem 5.4

### 5.6 The Difference-Amplifier Circuit


$$\frac{v_n - v_a}{R_a} + \frac{v_n - v_o}{R_b} + i_n = 0$$

$$v_n = v_p = \left( \frac{R_d}{R_c + R_d} \right) v_b$$

Substituting

$$v_o = \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)} v_b - \frac{R_b}{R_a} v_a$$
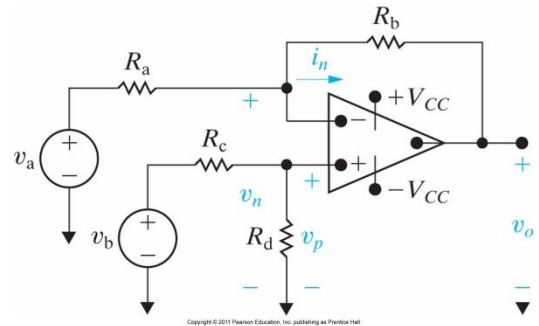
$$v_o = \frac{R_b}{R_a} (v_b - v_a) \quad \text{when} \quad \frac{R_a}{R_b} = \frac{R_c}{R_d}$$



Review Example 5.4 and Assessment Problem 5.5

### 5.7 A More Realistic Model for the Operational Amplifier

Differences from the ideal op amp model

1. A finite input resistance  $R_i$
2. A finite open-loop gain,  $A$
3. A non-zero output resistance  $R_o$

Cannot assume that  $i_p = i_n = 0$  or  $v_p = v_n$  or the general equation for the voltage transfer characteristics.



*Non-ideal inverting amplifier*

Node a

$$\frac{v_n - v_s}{R_s} + \frac{v_n}{R_i} + \frac{v_n - v_o}{R_f} = 0$$

Node b
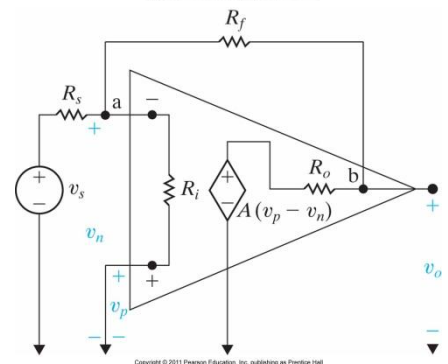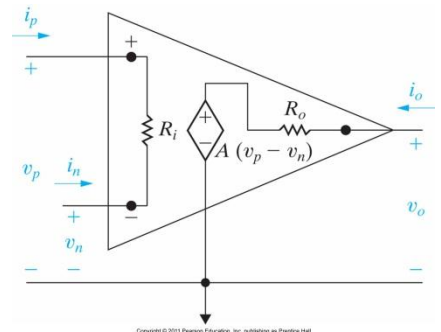
$$\frac{v_o - v_n}{R_f} + \frac{v_o - A(v_p - v_n)}{R_o} = 0$$



$$v_o = \frac{-A + \frac{R_o}{R_f}}{\frac{R_s}{R_f} \left( 1 + A + \frac{R_o}{R_f} \right) + \left( \frac{R_s}{R_i} + 1 \right) + \frac{R_o}{R_f}} v_s$$

## Chapter 5: The Operational Amplifier

Adding a load resistor  $R_L$

$$v_o = \frac{-A + \frac{R_o}{R_f}}{\frac{R_s}{R_f} \left(1 + A + \frac{R_o}{R_i} + \frac{R_o}{R_L}\right) + \left(\frac{R_s}{R_i} + 1\right) \left(\frac{R_o}{R_L} + 1\right) + \frac{R_o}{R_L}} v_s$$


*Non-ideal noninverting amplifier*

Node a

$$\frac{v_n}{R_s} + \frac{v_n - v_g}{R_g + R_i} + \frac{v_n - v_o}{R_f} = 0$$

Node b
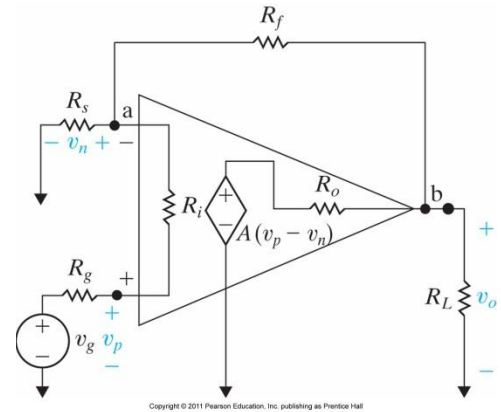
$$\frac{v_o - v_n}{R_f} + \frac{v_o}{R_L} + \frac{v_o - A(v_p - v_n)}{R_o} = 0$$



*See book for remaining derivation and Assessment Problem 5.6*