

## Chapter 8: Natural and Step Responses of the RLC Circuit


### 8.1 Introduction to the Natural Response of the Parallel RLC Circuit

Node Equation

$$\frac{v}{R} + \frac{1}{L} \int_0^t v D\tau + I_0 + C \frac{dv}{dt} = 0$$

Differentiating
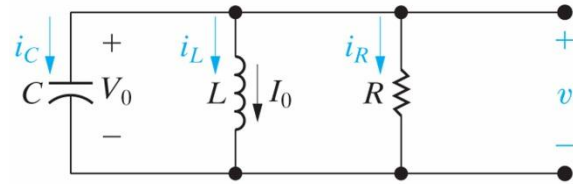
$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} + C \frac{d^2v}{dt^2} = \frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$



General solution for a second-order differential

$$\begin{aligned} \text{Assuming } V = Ae^{st} \quad \therefore \quad As^2e^{st} + \frac{As}{RC}e^{st} + \frac{Ae^{st}}{LC} &= 0 \\ Ae^{st} \left( s^2 + \frac{1}{RC}s + \frac{1}{LC} \right) &= 0 \end{aligned}$$

For the equation to be zero; the general form is:

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

Solving for the roots

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

And

$$s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Where

$$\alpha = \frac{1}{2RC} \text{ is the Neper frequency}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ is the resonant radian frequency}$$

**TABLE 8.1** Natural Response Parameters of the Parallel RLC Circuit

Parameter	Terminology	Value In Natural Response
$s_1, s_2$	Characteristic roots	$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$ $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$
$\alpha$	Neper frequency	$\alpha = \frac{1}{2RC}$
$\omega_0$	Resonant radian frequency	$\omega_0 = \frac{1}{\sqrt{LC}}$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Review Example 8.1 and Assessment Problem 8.1

## 8.2 The Forms of the Natural Response of the Parallel RLC Circuit

### *The Overdamped Voltage Response*

When  $\alpha^2 > \omega_0^2$  (distinct and real roots)

Overdamped: the voltage or current approaches its final value without oscillation

The natural response:

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

The process for finding the response

1. Find the roots of the equation by solving for  $s_1$  and  $s_2$  for the values of R, L and C.
2. Find  $v(0^+)$  and  $\frac{dv(0^+)}{dt}$  using circuit analysis.

Note:  $v(0^+)$  is the initial voltage in the capacitor &  $\frac{dv(0^+)}{dt}$  relates to the initial inductor current where  $i_c = C \frac{dv}{dt}$

3. Find  $A_1$  and  $A_2$  by solving the following equations simultaneously.

$$v(0^+) = A_1 + A_2 \quad \text{and} \quad \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = s_1 A_1 + s_2 A_2$$

4. Substitute these values into the characteristic equation to get the expression for  $v(t)$  for  $t \geq 0$ .

*Review Examples 8.2 & 8.3 and Assessment Problems 8.2 & 8.3*

### *The Underdamped Voltage Response*

When  $\omega_0^2 > \alpha^2$  (complex roots)

Underdamped: the voltage or current oscillates around its final value

Given

$$s_1 = -\alpha + \sqrt{-(\alpha^2 - \omega_0^2)} = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} = -\alpha + j\omega_d$$
$$s_2 = -\alpha - j\omega_d$$

Where  $\omega_d$  is the damped radian frequency and equals  $\sqrt{\omega_0^2 - \alpha^2}$ .

The natural response:

$$v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

Follow the same steps in the process to obtain the response as in the overdamped example except for the equations in step 3 use:

$$v(0^+) = V_0 = B_1 \quad \text{and} \quad \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = -\alpha B_1 + \omega_d B_2$$

Damping factor: ( $\alpha$ ) determines how quickly the oscillation will subside

*Review Example 8.4 and Assessment Problem 8.4*

### The Critically Damped Voltage Response

When  $\omega_0^2 = \alpha^2$  or  $\omega_0 = \alpha$

$$s_1 = s_2 = -\alpha = -\frac{1}{2RC}$$

The natural response:

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

Again, follow the same steps in the process to obtain the response except for the equations in step 3 use:

$$v(0^+) = V_0 = D_1 \quad \text{and} \quad \frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = D_1 - \alpha D_2$$

Review Example 8.5 and Assessment Problem 8.5

### 8.3 The Step Response of the Parallel RLC Circuit

KCL

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I$$

Where

$$v = L \frac{di_L}{dt} \quad \text{and} \quad \frac{dv}{dt} = L \frac{d^2 i_L}{dt^2}$$

Simplifying

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC} = s^2 + \frac{1}{RC} s + \frac{1}{LC}$$

Since the equation is similar to the natural response with the exception of the source, the general form for the given response is

$$i = I_f + \{\text{the form of the function for the natural response}\}$$

$$v = V_f + \{\text{the form of the function for the natural response}\}$$

Where  $I_f$  and  $V_f$  represent the final values of the response function

Review Examples 8.5 – 8.10 and Assessment Problem 8.6

### 8.4 The Natural and Step Response of the Series RLC Circuit



Node Equation

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_0^t i d\tau + V_0 = 0$$

Differentiating

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = \frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

The general form is:

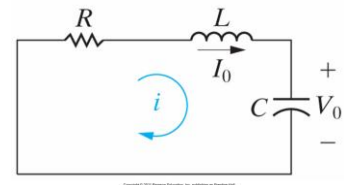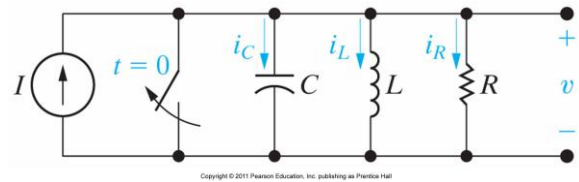

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

Solving for the roots

$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Where

$$\alpha = \frac{R}{2L} \text{ is the Neper frequency; } \omega_0 = \frac{1}{\sqrt{LC}} \text{ is the resonant radian frequency}$$

The current natural response for series RLC circuits:

$$\begin{aligned} i(t) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} \text{ (overdamped)} \\ i(t) &= B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t \text{ (underdamped)} \\ i(t) &= D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} \text{ (critically damped)} \end{aligned}$$

The voltage natural response for series RLC circuits:

$$\begin{aligned} v(t) &= V_f + A'_1 e^{s_1 t} + A'_2 e^{s_2 t} \text{ (overdamped)} \\ v(t) &= V_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t \text{ (underdamped)} \\ v(t) &= V_f + D'_1 t e^{-\alpha t} + D'_2 e^{-\alpha t} \text{ (critically damped)} \end{aligned}$$

Review Examples 8.11 & 8.12 and Assessment Problems 8.7 & 8.8

### Summarizing for Second Order circuit Responses

TABLE 8.2 The Response of a Second-Order Circuit is Overdamped, Underdamped, or Critically Damped

The Circuit is	When	Qualitative Nature of the Response
Overdamped	$\alpha^2 > \omega_0^2$	The voltage or current approaches its final value without oscillation
Underdamped	$\alpha^2 < \omega_0^2$	The voltage or current oscillates about its final value
Critically damped	$\alpha^2 = \omega_0^2$	The voltage or current is on the verge of oscillating about its final value

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

TABLE 8.3 In Determining the Natural Response of a Second-Order Circuit, We First Determine Whether it is Over-, Under-, or Critically Damped, and Then We Solve the Appropriate Equations

Damping	Natural Response Equations	Coefficient Equations
Overdamped	$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$	$x(0) = A_1 + A_2$ ; $dx/dt(0) = A_1 s_1 + A_2 s_2$
Underdamped	$x(t) = (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t}$	$x(0) = B_1$ ; $dx/dt(0) = -\alpha B_1 + \omega_d B_2$ , where $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$
Critically damped	$x(t) = (D_1 t + D_2) e^{-\alpha t}$	$x(0) = D_2$ , $dx/dt(0) = D_1 - \alpha D_2$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

TABLE 8.4 In Determining the Step Response of a Second-Order Circuit, We Apply the Appropriate Equations Depending on the Damping

Damping	Step Response Equations <sup>a</sup>	Coefficient Equations
Overdamped	$x(t) = X_f + A'_1 e^{s_1 t} + A'_2 e^{s_2 t}$	$x(0) = X_f + A'_1 + A'_2$ ; $dx/dt(0) = A'_1 s_1 + A'_2 s_2$
Underdamped	$x(t) = X_f + (B'_1 \cos \omega_d t + B'_2 \sin \omega_d t) e^{-\alpha t}$	$x(0) = X_f + B'_1$ ; $dx/dt(0) = -\alpha B'_1 + \omega_d B'_2$
Critically damped	$x(t) = X_f + D'_1 t e^{-\alpha t} + D'_2 e^{-\alpha t}$	$x(0) = X_f + D'_2$ ; $dx/dt(0) = D'_1 - \alpha D'_2$

<sup>a</sup> where  $X_f$  is the final value of  $x(t)$ .

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall