

Two-Port Parameters

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \Omega \quad z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \Omega \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \Omega \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \Omega \quad h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \Omega \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \text{ S}$$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \text{ S} \quad y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \text{ S} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \text{ S} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \text{ S} \quad g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} \text{ S} \quad g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0} \quad g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} \quad g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} \Omega$$

$$a_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad a_{12} = -\left. \frac{V_1}{I_2} \right|_{V_2=0} \Omega \quad a_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0} \text{ S} \quad a_{22} = -\left. \frac{I_1}{I_2} \right|_{V_2=0}$$

$$b_{11} = \left. \frac{V_2}{V_1} \right|_{I_1=0} \quad b_{12} = -\left. \frac{V_2}{I_1} \right|_{V_1=0} \Omega \quad b_{21} = \left. \frac{I_2}{V_1} \right|_{I_1=0} \text{ S} \quad b_{22} = -\left. \frac{I_2}{I_1} \right|_{V_1=0}$$

TABLE 18.1 Parameter Conversion Table

$$z_{11} = \frac{y_{22}}{\Delta y} = \frac{a_{11}}{a_{21}} = \frac{b_{22}}{b_{21}} = \frac{\Delta h}{h_{22}} = \frac{1}{g_{11}}$$

$$z_{12} = \frac{-y_{12}}{\Delta y} = \frac{\Delta a}{a_{21}} = \frac{1}{b_{21}} = \frac{h_{12}}{h_{22}} = \frac{g_{12}}{g_{11}}$$

$$z_{21} = \frac{-y_{21}}{\Delta y} = \frac{1}{a_{21}} = \frac{\Delta b}{b_{21}} = \frac{h_{21}}{h_{22}} = \frac{g_{21}}{g_{11}}$$

$$z_{22} = \frac{y_{11}}{\Delta y} = \frac{a_{22}}{a_{21}} = \frac{b_{11}}{b_{21}} = \frac{1}{h_{22}} = \frac{\Delta g}{g_{11}}$$

$$y_{11} = \frac{z_{22}}{\Delta z} = \frac{a_{22}}{a_{12}} = \frac{b_{11}}{b_{12}} = \frac{1}{h_{11}} = \frac{\Delta g}{g_{22}}$$

$$y_{12} = \frac{-z_{12}}{\Delta z} = \frac{-\Delta a}{a_{12}} = \frac{1}{b_{12}} = \frac{h_{12}}{h_{11}} = \frac{g_{12}}{g_{22}}$$

$$y_{21} = \frac{-z_{21}}{\Delta z} = \frac{-1}{a_{12}} = \frac{\Delta b}{b_{12}} = \frac{h_{21}}{h_{11}} = \frac{g_{21}}{g_{22}}$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Relationships for a reciprocal two-port circuit

$$z_{12} = z_{21} \quad a_{11}a_{22} - a_{12}a_{21} = \Delta a = 1 \quad h_{12} = -h_{21} \quad y_{12} = y_{21} \quad b_{11}b_{22} - b_{12}b_{21} = \Delta b = 1 \quad g_{12} = -g_{21}$$

TABLE 18.2 Terminated Two-Port Equations

z Parameters	y Parameters
$Z_{in} = z_{11} - \frac{z_{12}z_{21}}{z_{22} + Z_L}$	$Y_{in} = y_{11} - \frac{y_{12}y_{21}Z_L}{1 + y_{22}Z_L}$
$I_2 = \frac{-z_{21}V_g}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$	$I_2 = \frac{y_{21}V_g}{1 + y_{22}Z_L + y_{11}Z_g + \Delta y Z_g Z_L}$
$V_{Th} = \frac{z_{21}}{z_{11} + Z_g} V_g$	$V_{Th} = \frac{-y_{21}V_g}{y_{22} + \Delta y Z_g}$
$Z_{Th} = z_{22} - \frac{z_{12}z_{21}}{z_{11} + Z_g}$	$Z_{Th} = \frac{1 + y_{11}Z_g}{y_{22} + \Delta y Z_g}$
$\frac{I_2}{I_1} = \frac{-z_{21}}{z_{22} + Z_L}$	$\frac{I_2}{I_1} = \frac{y_{21}}{y_{11} + \Delta y Z_L}$
$\frac{V_2}{V_1} = \frac{z_{21}Z_L}{z_{11}Z_L + \Delta z}$	$\frac{V_2}{V_1} = \frac{-y_{21}Z_L}{1 + y_{22}Z_L}$
$\frac{V_2}{V_g} = \frac{z_{21}Z_L}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$	$\frac{V_2}{V_g} = \frac{y_{21}Z_L}{y_{12}y_{21}Z_g Z_L - (1 + y_{11}Z_g)(1 + y_{22}Z_L)}$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Relationships for two cascaded two-port circuits

$$a_{11} = a'_{11}a''_{11} + a'_{12}a''_{21} \quad a_{12} = a'_{11}a''_{12} + a'_{12}a''_{22} \quad a_{21} = a'_{21}a''_{11} + a'_{22}a''_{21} \quad a_{22} = a'_{21}a''_{12} + a'_{22}a''_{22}$$

Two-Port Parameters

General Equations

$$V_1 = z_{11}I_1 + z_{12}I_2 \quad I_1 = y_{11}V_1 + y_{12}V_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2 \quad I_2 = y_{21}V_1 + y_{22}V_2$$

$$V_1 = a_{11}V_2 - a_{12}I_2 \quad V_2 = b_{11}V_1 - b_{12}I_1$$

$$I_1 = a_{21}V_2 - a_{22}I_2 \quad I_2 = b_{21}V_1 - b_{22}I_1$$

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad I_1 = g_{11}V_1 + g_{12}I_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad V_2 = g_{21}V_1 + g_{22}I_2$$

TABLE 18.1 Parameter Conversion Table

$$y_{22} = \frac{z_{11}}{\Delta z} = \frac{a_{11}}{a_{12}} = \frac{b_{22}}{b_{12}} = \frac{\Delta h}{h_{11}} = \frac{1}{g_{22}}$$

$$a_{11} = \frac{z_{11}}{z_{21}} = \frac{y_{22}}{y_{21}} = \frac{b_{22}}{\Delta b} = \frac{\Delta h}{h_{21}} = \frac{1}{g_{21}}$$

$$a_{12} = \frac{\Delta z}{z_{21}} = \frac{1}{y_{21}} = \frac{b_{12}}{\Delta b} = \frac{h_{11}}{h_{21}} = \frac{g_{22}}{g_{21}}$$

$$a_{21} = \frac{1}{z_{21}} = \frac{\Delta y}{y_{21}} = \frac{b_{21}}{\Delta b} = \frac{h_{22}}{h_{21}} = \frac{g_{11}}{g_{21}}$$

$$a_{22} = \frac{z_{22}}{z_{21}} = \frac{y_{11}}{y_{21}} = \frac{b_{11}}{\Delta b} = \frac{1}{h_{21}} = \frac{\Delta g}{g_{21}}$$

$$b_{11} = \frac{z_{22}}{z_{12}} = \frac{y_{11}}{y_{12}} = \frac{a_{22}}{\Delta a} = \frac{1}{h_{12}} = \frac{\Delta g}{g_{12}}$$

$$b_{12} = \frac{\Delta z}{z_{12}} = \frac{-1}{y_{12}} = \frac{a_{12}}{\Delta a} = \frac{h_{11}}{h_{12}} = \frac{g_{22}}{g_{12}}$$

$$g_{11} = \frac{1}{z_{11}} = \frac{\Delta y}{y_{22}} = \frac{a_{21}}{a_{11}} = \frac{b_{21}}{b_{22}} = \frac{h_{22}}{\Delta h}$$

$$g_{12} = \frac{-z_{12}}{z_{11}} = \frac{-\Delta a}{a_{11}} = \frac{1}{b_{22}} = \frac{h_{12}}{\Delta h}$$

$$g_{21} = \frac{z_{21}}{z_{11}} = \frac{y_{21}}{a_{11}} = \frac{1}{b_{22}} = \frac{\Delta b}{\Delta h}$$

$$g_{22} = \frac{\Delta z}{z_{11}} = \frac{1}{y_{22}} = \frac{a_{12}}{a_{11}} = \frac{b_{12}}{b_{22}} = \frac{h_{11}}{\Delta h}$$

$$\Delta z = z_{11}z_{22} - z_{12}z_{21}$$

$$\Delta y = y_{11}y_{22} - y_{12}y_{21}$$

$$\Delta a = a_{11}a_{22} - a_{12}a_{21}$$

$$\Delta b = b_{11}b_{22} - b_{12}b_{21}$$

$$\Delta h = h_{11}h_{22} - h_{12}h_{21}$$

$$\Delta g = g_{11}g_{22} - g_{12}g_{21}$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Relationships for a symmetric two-port circuit

$$z_{11} = z_{22} \quad h_{11}h_{22} - h_{12}h_{21} = \Delta h = 1 \quad a_{11} = a_{22}$$

$$y_{11} = y_{22} \quad g_{11}g_{22} - g_{12}g_{21} = \Delta g = 1 \quad b_{11} = b_{22}$$

TABLE 18.2 Terminated Two-Port Equations

a Parameters	b Parameters
$Z_{in} = \frac{a_{11}Z_L + a_{12}}{a_{21}Z_L + a_{22}}$	$Z_{in} = \frac{b_{22}Z_L + b_{12}}{b_{21}Z_L + b_{11}}$
$I_2 = \frac{-V_g}{a_{11}Z_L + a_{12} + a_{21}Z_g Z_L + a_{22}Z_g}$	$I_2 = \frac{-V_g \Delta b}{b_{11}Z_g + b_{21}Z_g Z_L + b_{22}Z_L + b_{12}}$
$V_{Th} = \frac{V_g}{a_{11} + a_{21}Z_g}$	$V_{Th} = \frac{V_g \Delta b}{b_{22} + b_{21}Z_g}$
$Z_{Th} = \frac{a_{12} + a_{22}Z_g}{a_{11} + a_{21}Z_g}$	$Z_{Th} = \frac{b_{11}Z_g + b_{12}}{b_{21}Z_g + b_{22}}$
$\frac{I_2}{I_1} = \frac{-1}{a_{21}Z_L + a_{22}}$	$\frac{I_2}{I_1} = \frac{-\Delta b}{b_{11} + b_{21}Z_L}$
$\frac{V_2}{V_1} = \frac{Z_L}{a_{11}Z_L + a_{12}}$	$\frac{V_2}{V_1} = \frac{\Delta b Z_L}{b_{12} + b_{22}Z_L}$
$\frac{V_2}{V_g} = \frac{Z_L}{(a_{11} + a_{21}Z_g)Z_L + a_{12} + a_{22}Z_g}$	$\frac{V_2}{V_g} = \frac{\Delta b Z_L}{b_{12} + b_{11}Z_g + b_{22}Z_L + b_{21}Z_g Z_L}$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall