

# ECEN 4856

Lecture 4: Lab 2 Discussion

## VHDL Precedence

Table A.1 The VHDL operators.

	Operator Class	Operator
Highest precedence	Miscellaneous	**, ABS, NOT
	Multiplying	*, /, MOD, REM
	Sign	+, -
	Adding	+, -, &
	Relational	=, / =, <, <=, >, >=
Lowest precedence	Logical	AND, OR, NAND, NOR, XOR, XNOR

Example,

x1 AND x2 OR x3 AND x4

does not have mean

x1x2 + x3x4

Because AND does not have precedence over OR. To have the desired meaning, it must be written as

(x1 AND x2) OR (x3 AND x4)

## VHDL Review – Case Statements

(Page 358 in textbook)

**Case statements** Executes one of several sequences of statements, based on the value of a single expression. The syntax is as follows:

```

case expression is
  when choices =>
    sequential statements
  when choices =>
    sequential statements
    -- branches are
allowed
  [when others => sequential
statements ]
end case;
```

## Case Example – Selecting a grade

```

library ieee;
use ieee.std_logic_1164.all;
entity GRD_201 is
  port (VALUE: in integer range 0 to 100;
        A, B, C, D: out bit);
end GRD_201;
architecture behav_grd of GRD_201 is
begin
  process (VALUE)
  A <= '0';
  B <= '0';
  C <= '0';
  D <= '0';
  F <= '0';
  begin
    case VALUE is
      when 51 to 60 => D <= '1';
      when 61 to 70 | 71 to 75 => C <= '1';
      when 76 to 85 => B <= '1';
      when 86 to 100 => A <= '1';
      when others => F <= '1';
    end case;
  end process;
end behav_grd;
```

The "/" symbol used to show how multiple values can be on a line.

## Case Example – 4 to 1 MUX

```

entity MUX_4_1 is
  port ( SEL: in std_logic_vector(2 downto 1);
        A, B, C, D: in std_logic;
        Z: out std_logic);
end MUX_4_1;
architecture behav_MUX41 of MUX_4_1 is
begin
  PR_MUX: process (SEL, A, B, C, D)
  begin
    case SEL is
      when "00" => Z <= A;
      when "01" => Z <= B;
      when "10" => Z <= C;
      when "11" => Z <= D;
      when others => Z <= 'X';
    end case;
  end process PR_MUX;
end behav_MUX41;
```

## VHDL Review - Component

**Component:** a sub-circuit of a VHDL file, that either must be a previously defined entity in a library or entity within the VHDL file. Syntax for calling the component:

```

component component_name is
  port (port_signal_names: mode type;
        port_signal_names: mode type;
        :
        port_signal_names: mode type);
end component [component_name];
begin
  port map [list of actual signals]
```

## Example – 4 Bit Adder

```

-- Example of a four bit adder
library ieee;
use ieee.std_logic_1164.all;

-- definition of a full adder
entity FULLADDER is
  port (a, b, c: in std_logic;
        sum, carry: out std_logic);
end FULLADDER;

architecture fulladder_behav of FULLADDER is
begin
  sum <= (a xor b) xor c;
  carry <= (a and b) or (c and (a xor b));
end fulladder_behav;
(Continue on the right column)

-- 4-bit adder
library ieee;
use ieee.std_logic_1164.all;
entity FOURBITADD is
  port (a, b: in std_logic_vector(3 downto 0);
        Cin: in std_logic;
        sum: out std_logic_vector(4 downto 0);
        Cout, V: out std_logic);
end FOURBITADD;

architecture fouradder_structure of FOURBITADD is
  signal c: std_logic_vector(4 downto 0);
  component FULLADDER
    port (a, b, c: in std_logic;
          sum, carry: out std_logic);
  end component;
begin
  FA0: FULLADDER
  port map (a(0), b(0), Cin, sum(0), c(1));
  FA1: FULLADDER
  port map (a(1), b(1), C(1), sum(1), c(2));
  FA2: FULLADDER
  port map (a(2), b(2), c(2), sum(2), c(3));
  FA3: FULLADDER
  port map (a(3), b(3), C(3), sum(3), c(4));
  V <= c(3) xor c(4);
  Cout <= c(4);
end fouradder_structure;
end fouradder_structure;

```

## Lab #2

- Due Thursday 9/18/14
  - Hardcopy of team lab report
- Total of 6 parts
  - Knowledge gained from previous parts is utilized in later parts
  - Include a copy of your VHDL code for each part
  - Document and describe what was learned
- Combines Lab1 with the use of 7-segment display
  - A total of 6 are available on DE2 board
  - Can represent digits 0-9 and hex letters A-F

## 7-Segment Display Pin out

 


Figure 4-10 Connections between the 7-segment display HEX0 and Cyclone IV E FPGA

Note: Applying a low logic level to a segment will light it up and applying a high logic level turns it off.

## References

- VHDL Primer: [http://www.seas.upenn.edu/~ese171/vhdl/vhdl\\_primer.html](http://www.seas.upenn.edu/~ese171/vhdl/vhdl_primer.html)
- *Fundamentals of Digital Logic with VHDL Design*: Stephen Brown and Zvonko Vranesic ISBN 978-0-07-352953-0