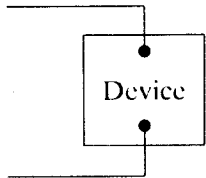


(Please show ALL of your work and label the circuits to achieve maximum credit)

1. [10 POINTS]

Five coulombs of charge pass through the element (device) from top to bottom in 10 seconds. The element delivers 120 J of energy during the 10 seconds. Determine the values for v_t and i_t .



$q = 5 \text{ C}$ $t = 10 \text{ s}$

$w = 120 \text{ J}$ $t = 10 \text{ s}$

$v = \frac{dw}{dq} = \frac{120}{5} = 24 \text{ V}$


$i = \frac{dq}{dt} = \frac{5}{10} = 0.5 \text{ A}$

2. [15 POINTS]

Given that the following circuit is valid:

a) Using Ohm's Law find i_1

$i_1 = \frac{6}{3} = 2 \text{ A}$

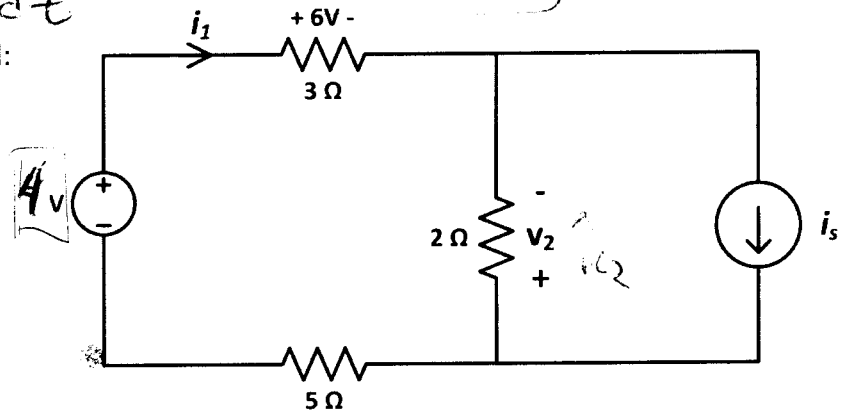

b) Find v_2 using KVL

$-4 + 6 + v_2 + 5i_1 = 0$

$v_2 = 2 + 5(2) = 12 \text{ V}$

c) Find i_s using KCL

$-i_1 + i_s + i_2 = 0$

$i_2 = \frac{v_2}{2}$


$i_2 = 2 + \frac{12}{2}$

$i_2 = 8 \text{ A}$

~~Handwritten scribbles and crossed-out work.~~

3. [25 POINTS] Using KCL, KVL and Ohm's Law:

a. Find i_2

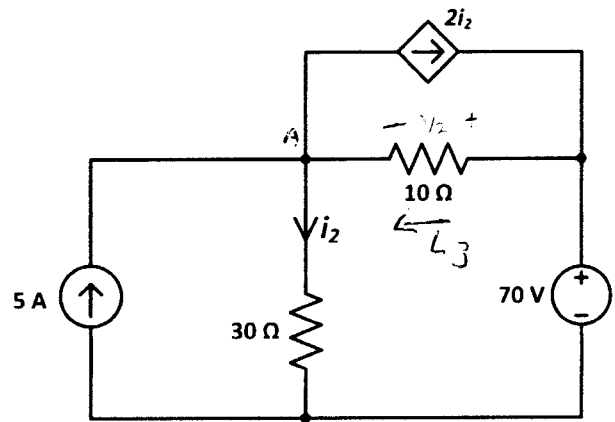

KCL A

$$-5 + i_2 + 2i_2 - i_3 = 0$$

$$3i_2 - 5 = i_3$$

KVL

$$v_3 = 10i_3$$

$$v_3 = 30i_2$$

$$10i_3 + 30i_2 - 70 = 0$$

sub

$$10(3i_2 - 5) + 30i_2 = 70$$

$$30i_2 - 50 + 30i_2 = 70$$

$$60i_2 = 120$$

$$i_2 = 2 \text{ A}$$


b. Find the power absorbed by the 10Ω resistor

$$P_{10} = i_2^2 R = (3(2) - 5)^2 10$$

$$P_{10} = 10 \text{ W}$$

4. [25 POINTS]

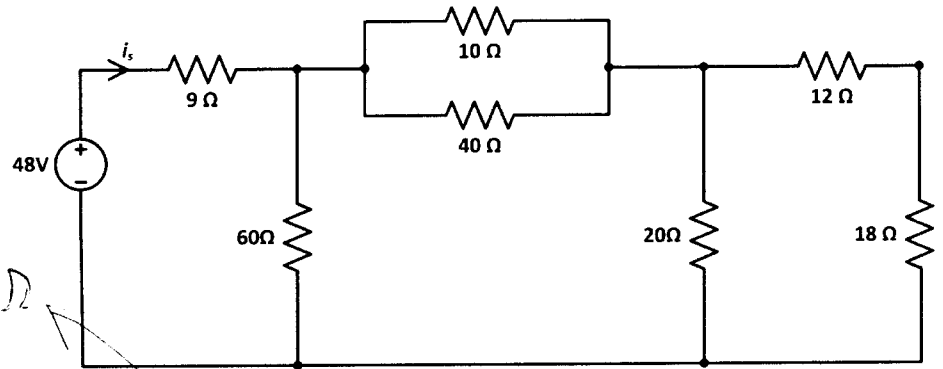a) Find the equivalent resistance as seen by the source.



$$12 + 18 = 30 \Omega$$





$$20 \parallel 30 = \frac{600}{50} = 12 \Omega$$

$$10 \parallel 40 = \frac{400}{50} = 8 \Omega$$

$$8 + 12 = 20 \Omega$$

$$20 \parallel 60 = \frac{1200}{80} = 15 \Omega$$

$$R_{eq} = 9 + 15 = 24 \Omega$$

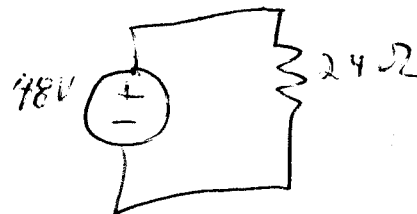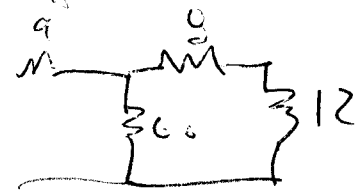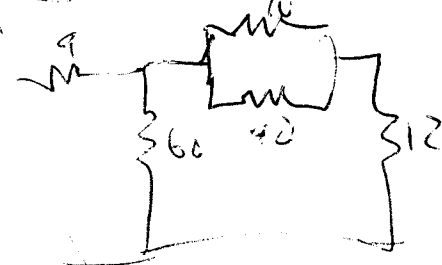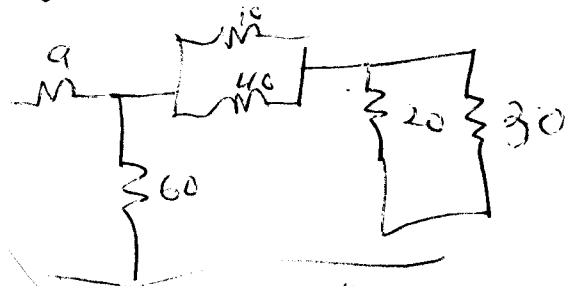

b) Determine the power delivered by the 48V source.

$$P = V_s I_s = 48 \left(\frac{48}{24} \right) = 96 \text{ W}$$

$$I_s = \frac{48}{24}$$

