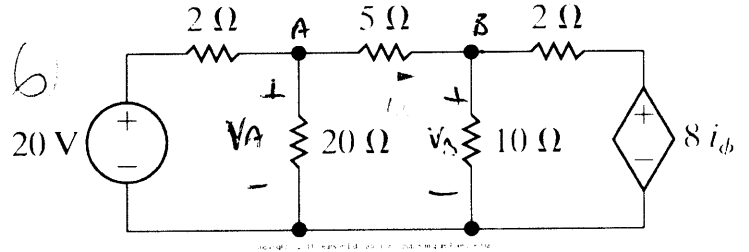


(Please show ALL of your work and label the circuits to achieve maximum credit)

1. [25 POINTS] Use the node-voltage method to determine the current through the 5 Ω resistor ( $i_\phi$ ). Label your nodes on the circuit

$$i) \frac{V_A - 20}{2} + \frac{V_A - V_B}{5} + \frac{V_A}{20} = 0$$



$$10V_A - 200 + 4V_A - 4V_B + V_A = 0$$

$$15V_A - 4V_B = 200$$

$$ii) \frac{V_B - V_A}{5} + \frac{V_B}{10} + \frac{V_B - 8I_\phi}{2} = 0$$

$$iii) I_\phi = \frac{V_A - V_B}{5}$$

$$2V_B - 2V_A + V_B + 5V_B - 40\left(\frac{V_A - V_B}{5}\right) = 0$$

$$8V_B - 2V_A - 8V_A + 8V_B = 0$$

$$16V_B - 10V_A = 0$$

$$V_A = 1.6V_B = 16V$$

$$15(1.6)V_B - 4V_B = 200$$

$$24V_B - 4V_B = 200$$


$$20V_B = 200$$

$$V_B = 10V$$

$$I_\phi = \frac{16 - 10}{5} = \frac{6}{5}$$

$$I_\phi = 1.2 A$$

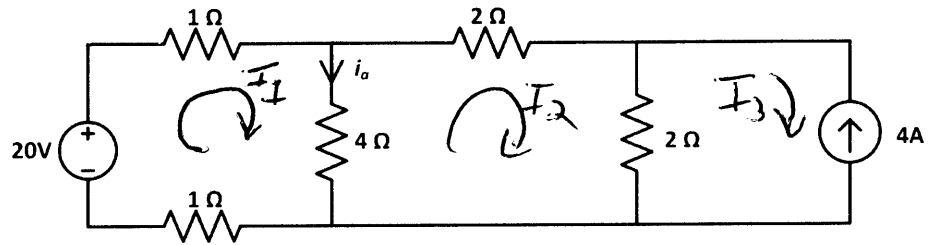2. [25 POINTS] Use Mesh-current analysis to determine the current  $i_a$ . Show your mesh loops on the figure.



$$i) -20 + I_1 + 4(I_1 - I_2) + I_1 = 0$$

$$6I_1 - 4I_2 = 20$$

$$ii) 4(I_2 - I_1) + 2I_2 + 2(I_2 - I_3) = 0$$

$$-4I_1 + 8I_2 - 2I_3 = 0$$

$$iii) I_3 = -4A$$

$$6I_1 - 4I_2 = 20$$

$$-4I_1 + 8I_2 = -8$$

$$12I_1 - 8I_2 = 40$$

$$\Rightarrow -4I_1 + 8I_2 = -8$$

$$8I_1 = 32$$

$$I_1 = 4A$$


$$-4I_2 = 20 - 6(4)$$

$$I_2 = \frac{-4}{-4} = 1A$$




$$i_a = I_1 - I_2$$

$$i_a = 4 - 1 = 3A$$

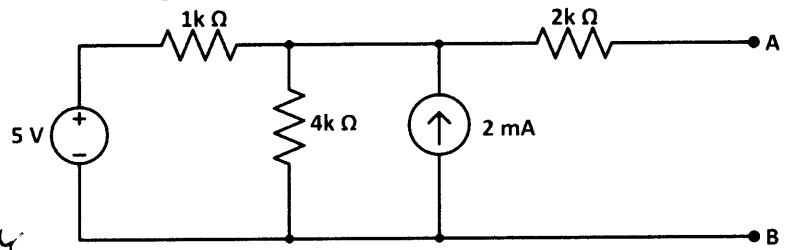
3. [25 POINTS] Find the Thevenin and Norton equivalent circuits with respect to terminals A-B.



$1k \parallel 4k = 0.8k$  (3)  
 0.8

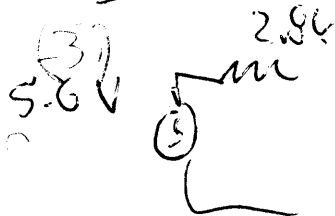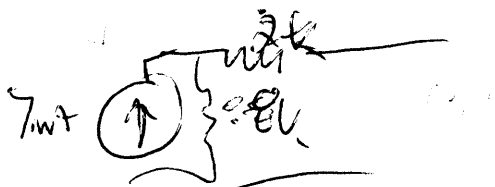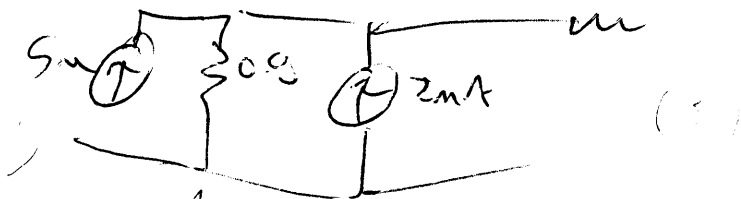


$\frac{5.6}{2.9k} = 2mA$  (3)

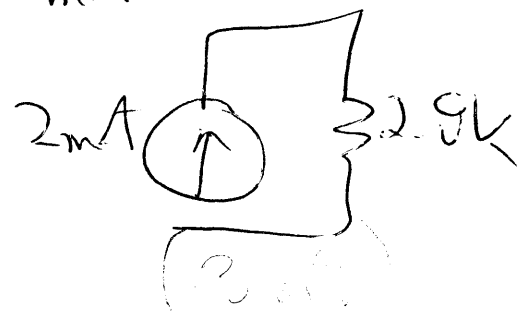

1. Find thevenin voltage  
 2. Find thevenin resistance  
 3. Find the Norton current  
 4. Find the Norton resistance  
 5. Draw the equivalent circuit

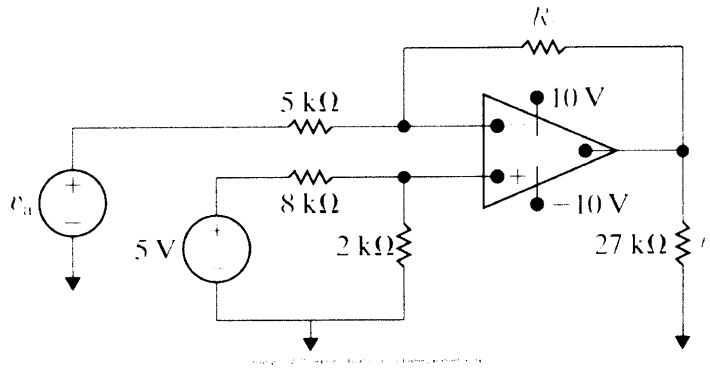4. [25 POINTS] Given that this is an ideal Op-amp and  $R_f = 20k\Omega$  and  $v_o = 1V$

- Find  $v_o$
- What is the range of  $v_o$  that allows the op amp to operate in its linear range?



$$V_p = V_N \quad L_p = L_n = 0$$

$$V_o = \left( \frac{2k}{10k} \right) 5 = 1V$$

$$\frac{V_N - V_A}{5k} + \frac{V_N - V_o}{2k} + \overset{0}{V_N} = 0$$

~~$$V_N = 2V_A$$~~

$$4V_N - 4V_A + V_N - V_o = 0$$

$$V_o = 5V_N - 4V_A$$

$$V_o = 5 - 4 = 1V$$

$$b) \quad 10 = 5 - 4V_A$$

$$-4V_A = 5$$

$$V_A = -\frac{5}{4} = -1.25V$$

$$-10 = 5 - 4V_A$$

$$-15 = -4V_A$$

$$V_A = \frac{15}{4} = 3.75V$$

$$-1.25V \leq V_A \leq 3.75V$$