

Test #2 ECEN 2632 F-2013 P. Munro Name: \_\_\_\_\_


20 pts each.

① Solve these simultaneous equations for  $v_1$  and  $v_2$ .

$$2 = 3v_1 - 4v_2$$


$$0 = -v_1 + 8v_2$$

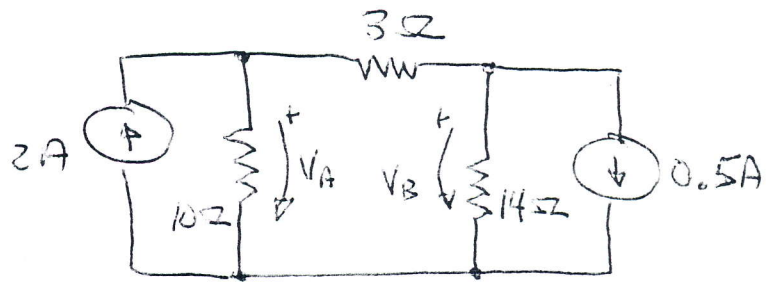② Write the nodal method equations needed to find  $V_A$  and  $V_B$ . Put in ready to solve form but do not solve.




3

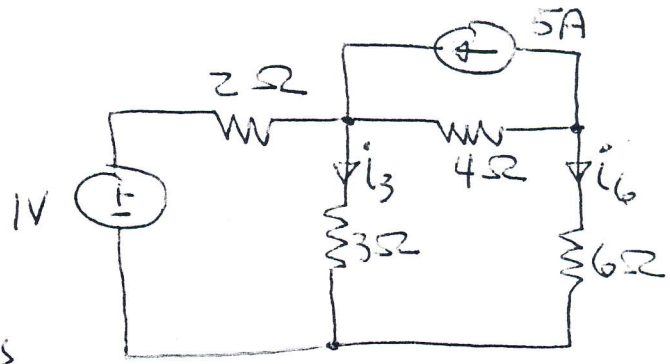- a) Write the mesh equations. Do not solve.
- b) Write  $i_3$  and  $i_6$  in terms of your mesh currents.




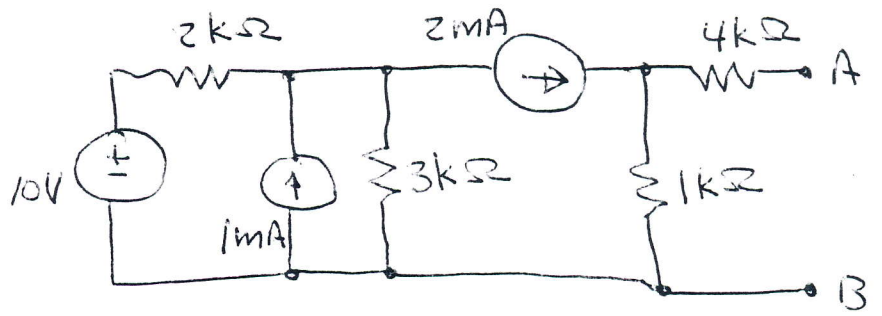④ Find and draw  
the Thevenin and  
the Norton circuits  
for A-B.




5

Use superposition  
to find  $i_1$ .

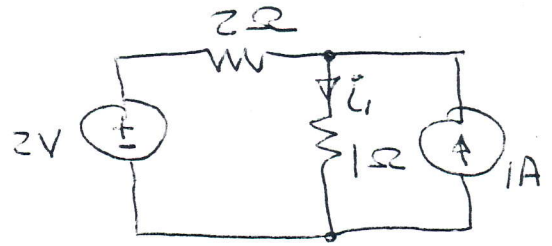

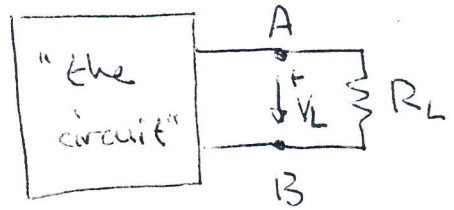⑥ The circuit has  
 $R_{\text{Thev}} = 10 \Omega$ . Also, when  
 $R_L = \infty$ ,  $V_L = 5 \text{ V}$ .



- Find  $R_L$  to make  $P_L$  a maximum.
- Draw the Thevenin equivalent for the circuit.