
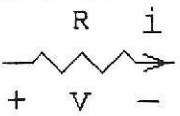
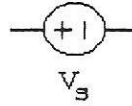
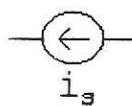


SOME USEFUL FACTS

<p><u>Resistor & Ohm's Law</u></p>  <p>$v = Ri$ or $i = Gv$, $G = \frac{1}{R}$</p>	<p><u>Voltage Source</u></p>  <p>Voltage v_s is known. Current is unknown.</p>	<p><u>Current Source</u></p>  <p>Current i_s is known. Voltage is unknown.</p>
--	--	--


Power & the Passive Sign Convention [PSC]

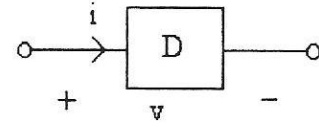Power into a device [or absorbed by the device]: $P_{in} = vi$
[using the passive sign convention]



Power to a resistor: $p_R = vi = i^2R = \frac{v^2}{R}$ $p = \frac{dw}{dt}$

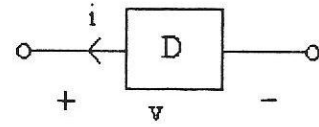Power out of a device [or delivered by the device]: $P_{out} = vi$
[not using the passive sign convention]



Kirchhoff's Laws

KVL: algebraic sum of voltages around a loop equals zero; or sum of all voltage drops around a loop equals zero.

KCL: algebraic sum of currents at a node equals zero; or sum of all currents leaving a node equals zero.

Series & Parallel Combinations

Voltage sources: in series: add the voltage waveforms
 in parallel: the voltages must be the same

Resistance in Parallel

$$\frac{1}{R_{eq}} = \sum_{i=1}^k \frac{1}{R_i} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_k}$$

Current sources: in parallel: add the current waveforms
 in series: the currents must be the same

ADD resistances in SERIES $R_{eq} = \sum_{i=1}^k R_i = R_1 + R_2 + \dots + R_k$

Two resistors in parallel:

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

ADD conductances in PARALL $G_{eq} = \sum_{i=1}^k G_i = G_1 + G_2 + \dots + G_k$

Voltage divider $v_j = iR_j = \left(\frac{R_j}{R_{eq}}\right)v$

Current divider $i_j = \frac{v}{R_j} = \left(\frac{R_{eq}}{R_j}\right)i$

$$v = \frac{dw}{dq}; \quad i = \frac{dq}{dt}$$

Prefix	Symbol	Power
atto	a	10^{-18}
femto	f	10^{-15}
pico	p	10^{-12}
nano	n	10^{-9}
micro	μ	10^{-6}
milli	m	10^{-3}
centi	c	10^{-2}
deci	d	10^{-1}
deka	da	10
hecto	h	10^2
kilo	k	10^3
mega	M	10^6
giga	G	10^9
tera	T	10^{12}

TABLE 1.3 Standardized Prefixes to Signify Powers of 10

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall