
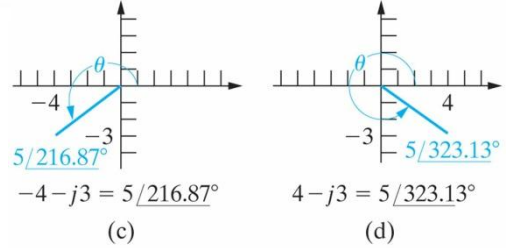
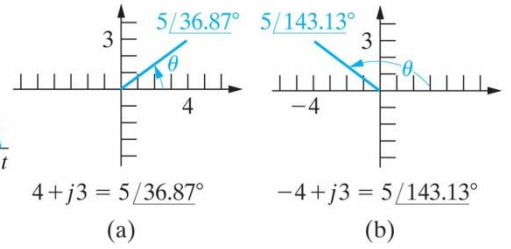


TABLE 9.1 Impedance and Reactance Values

| Circuit Element | Impedance | Reactance |
|-----------------|------------------|---------------|
| Resistor | R | – |
| Inductor | $j\omega L$ | ωL |
| Capacitor | $j(-1/\omega C)$ | $-1/\omega C$ |

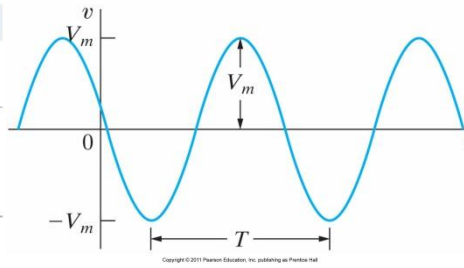

$$V = ZI \quad M = k\sqrt{L_1 L_2} \quad L = N^2 \phi$$

$$w(t) = \frac{L_1 i_1^2}{2} + \frac{L_2 i_2^2}{2} \pm i_1 i_2 M$$

$$v = V_m \cos(\omega t + \phi) \quad f = \frac{\omega}{2\pi} \quad V_{eff} = \frac{V_m}{\sqrt{2}}$$

Rectangular to Polar conversion

$$V = A + jB = \sqrt{A^2 + B^2} \angle \left(\tan^{-1} \frac{B}{A} \right)^\circ$$

Polar to Rectangular conversion

$$V = V_m \angle \phi^\circ = V_m \cos \phi + jV_m \sin \phi \text{ (Note that } V_m \text{ is a magnitude and should be positive, thus angle differs)}$$

Complex Arithmetic

Addition/Subtraction – must be in rectangular coordinates; combine real terms and imaginary terms. Ex. $(A_1 + jB_1) + (A_2 + jB_2) = (A_1 + A_2) + j(B_1 + B_2)$

Multiplication

Rectangular coordinates; distribute (FOIL)
Polar coordinates; multiply the magnitudes and add the angles

Division

Polar coordinates; divide the magnitudes and subtract the angles
Rectangular coordinates; multiply the denominator and numerator by the complex conjugate of the denominator, then simplify

Complex Number Identities $j^2 = -1$ and $\frac{1}{j} = -j$

Average Power

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = V_{eff} I_{eff} \cos(\theta_v - \theta_i) = |\vec{I}_{eff}|^2 R = \frac{1}{2} I_m^2 R = \frac{|\vec{V}_{eff}|^2}{R}$$

Reactive Power

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = V_{eff} I_{eff} \sin(\theta_v - \theta_i) = |\vec{I}_{eff}|^2 X = \frac{1}{2} I_m^2 X = \frac{|\vec{V}_{eff}|^2}{X}$$

Complex power $S = P + jQ$

$$S = \frac{1}{2} V_m I_m \angle (\theta_v - \theta_i) = V_{eff} I_{eff} \angle (\theta_v - \theta_i) = \vec{V}_{eff} \vec{I}_{eff}^* = \frac{1}{2} \vec{V} \vec{I}^* = |\vec{I}_{eff}|^2 Z$$

Apparent Power $|S| = \sqrt{P^2 + Q^2}$

Power factor $pf = \cos(\theta_v - \theta_i)$


Lagging power factor: implies that the current lags the voltage – hence *inductive load*

Leading power factor: implies that the current leads the voltage – hence *capacitive load*

Voltage Divider

$$v_1 = iR_1 = \left(\frac{R_1}{R_1 + R_2} \right) v_s$$
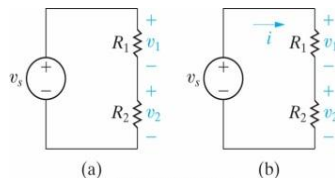
$$v_2 = iR_2 = \left(\frac{R_2}{R_1 + R_2} \right) v_s$$



Current Divider

$$i_1 = \left(\frac{R_2}{R_1 + R_2} \right) i_s$$

$$i_2 = \left(\frac{R_1}{R_1 + R_2} \right) i_s$$

